

Digital Filtering using C8051F020



Course: **Bioelectronics**

Team ID: 01

Team members:

<i>Name</i>	SEC	BN	Seating Number
<i>Rawan Sayed</i>	1	30	53030
<i>Sara Adel</i>	1	35	53035
<i>AlZahraa Eid</i>	1	16	53016
<i>Ahmed Adel Ahmed</i>	1	06	53006
<i>Kirollos Dawood</i>	2	15	53060

Submitted to Dr. Ahmed Ehab

ABSTRACT

Real-time digital filtering module receives noisy analog signals simultaneously via its channels and have 2 types of digital filter. After filtration, digital signals shall be converted into analog again and accessed via the C8051F020 pins .

Table of Contents

INTRODUCTION..... 1

CIRCUIT SCHEMATIC..... 1

CIRCUIT DIAGRAM 2

DESIGN DESCRIPTION..... 2

DESCRIPTION FOR DIGITAL FILTERS USED ALONG WITH EQUATIONS 6

List of Figures


FIGURE1 :CIRCUIT SCHEMATIC	1
FIGURE2 :CIRCUIT DIAGRAM.....	2
FIGURE3 :WEIGHTED SUMMER.....	2
FIGURE4 :USED SIGNALS	3
FIGURE5 : ADC	3
FIGURE6 :MICROCONTROLLER C8051F020	4
FIGURE7 : DAC	4
FIGURE8 :OUTPUT WITHOUT FILTRATION	5
FIGURE9 :OUTPUT WITH FILTRATION	5
FIGURE10 :FILTRATION EQUATIONS	6
FIGURE11 : FILTRATION COEFFICIENTS	6

Introduction

We have 2 signals so we use 2 weighted summer each one used to add three sinusoidal waves to enter to ADC then to our microcontroller C8051F020

After that, we use low pass filter for signal one and high pass filter for signal two and finally we enter the both signals to DAC

Circuit schematic

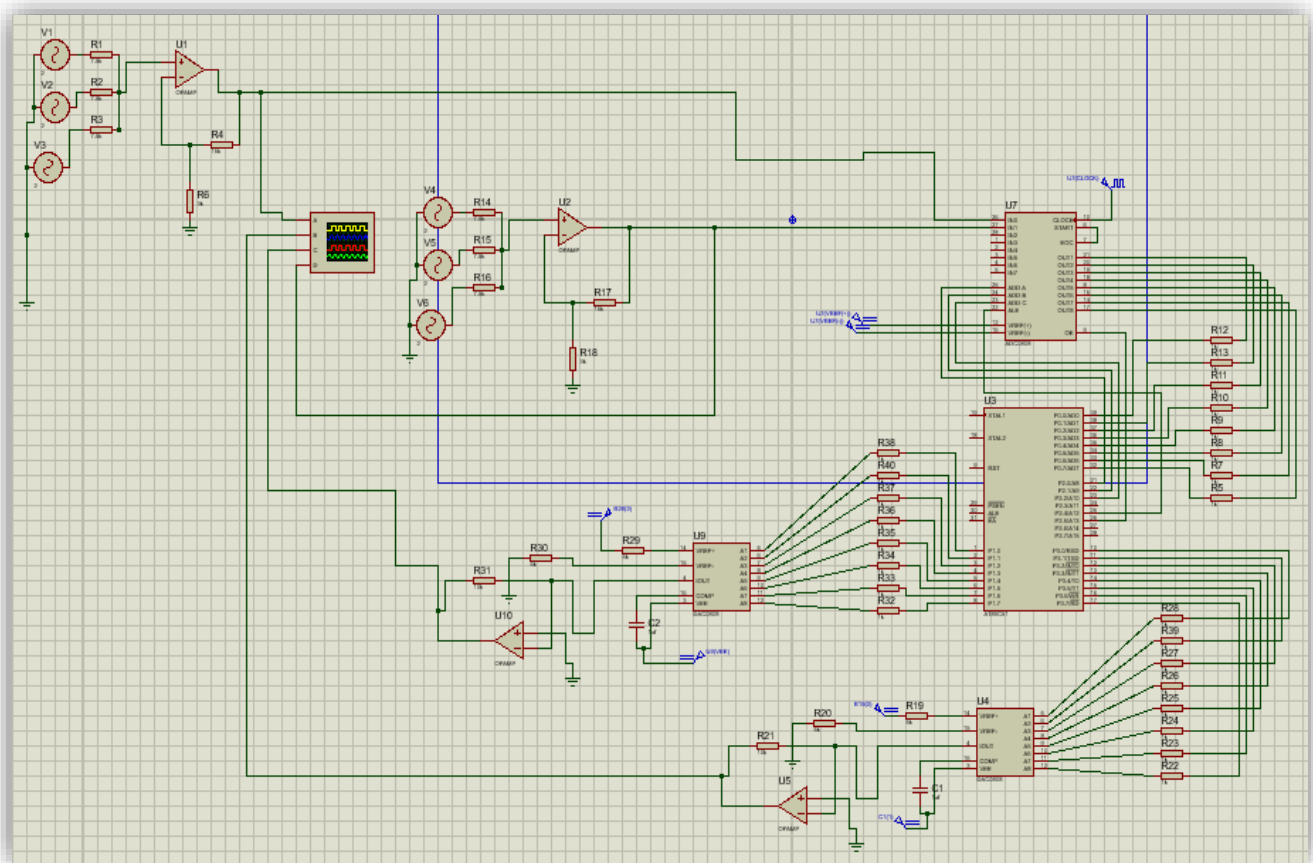

Circuit Diagram

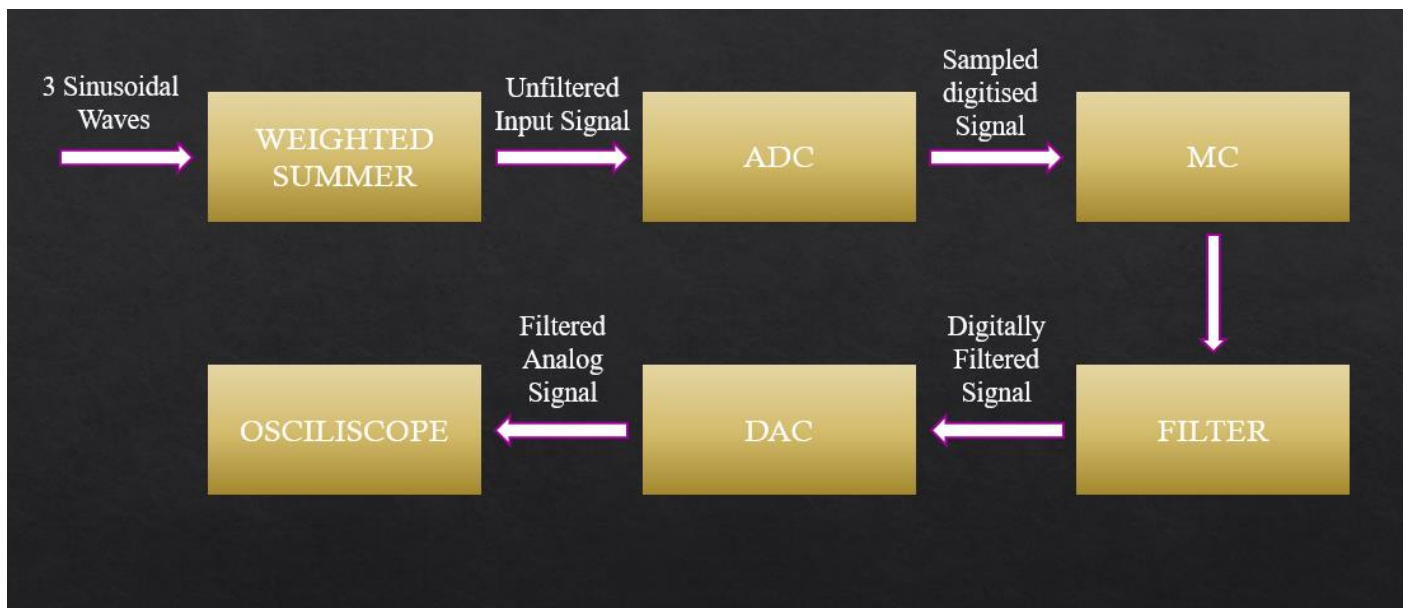


Figure2 :Circuit Diagram

Design description

✚ Weighted Summer

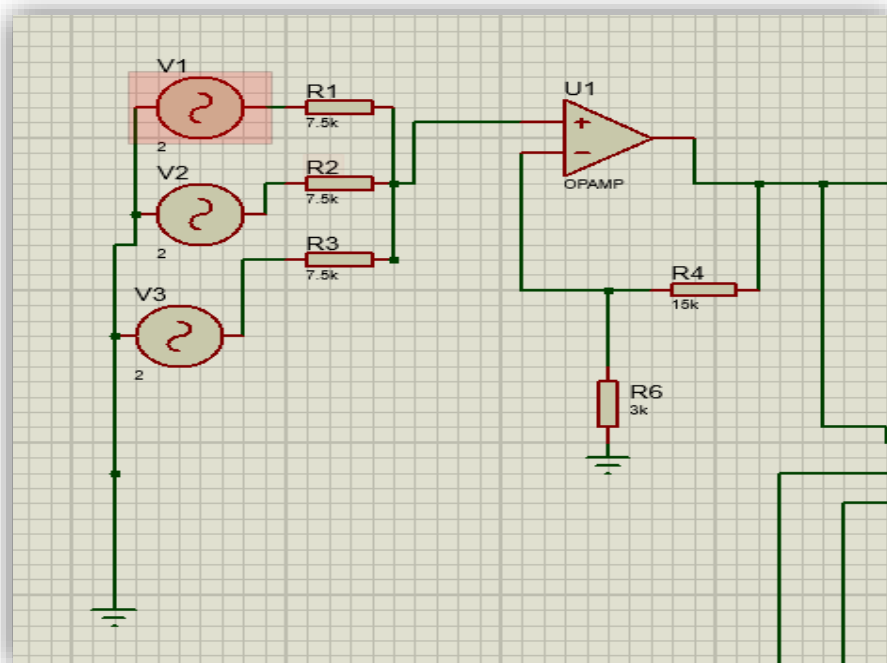


Figure3 :Weighted Summer

✚ Our 2 used signals after weighted summer at two different channels

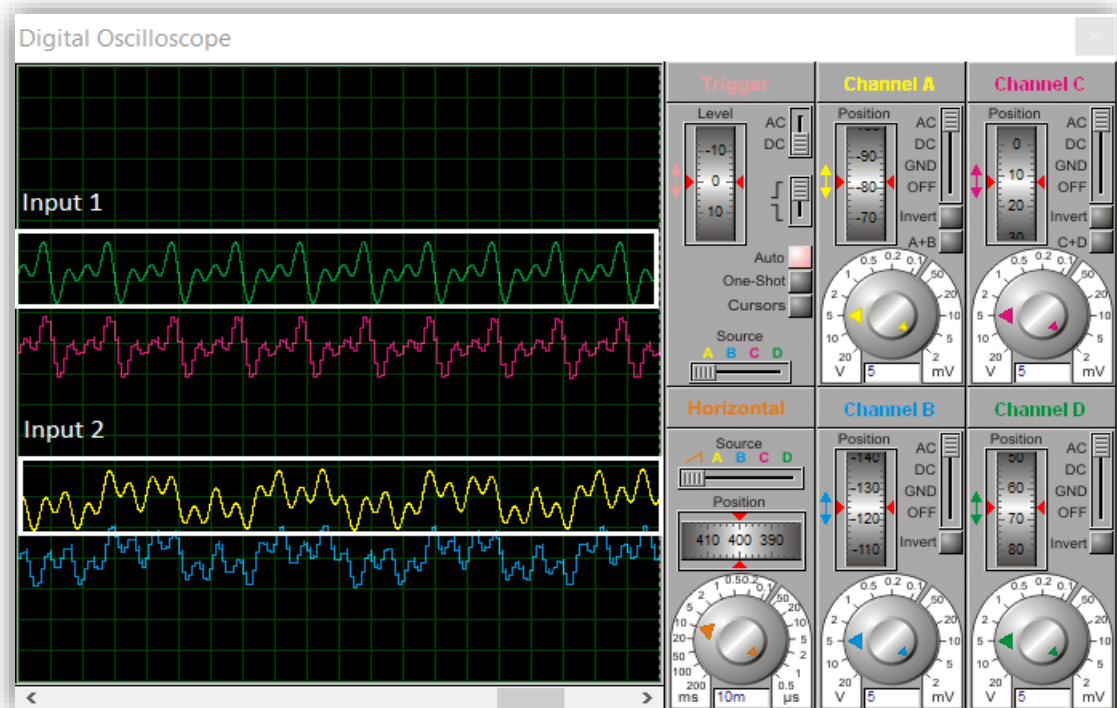


Figure4:Used Signals

✚ ADC

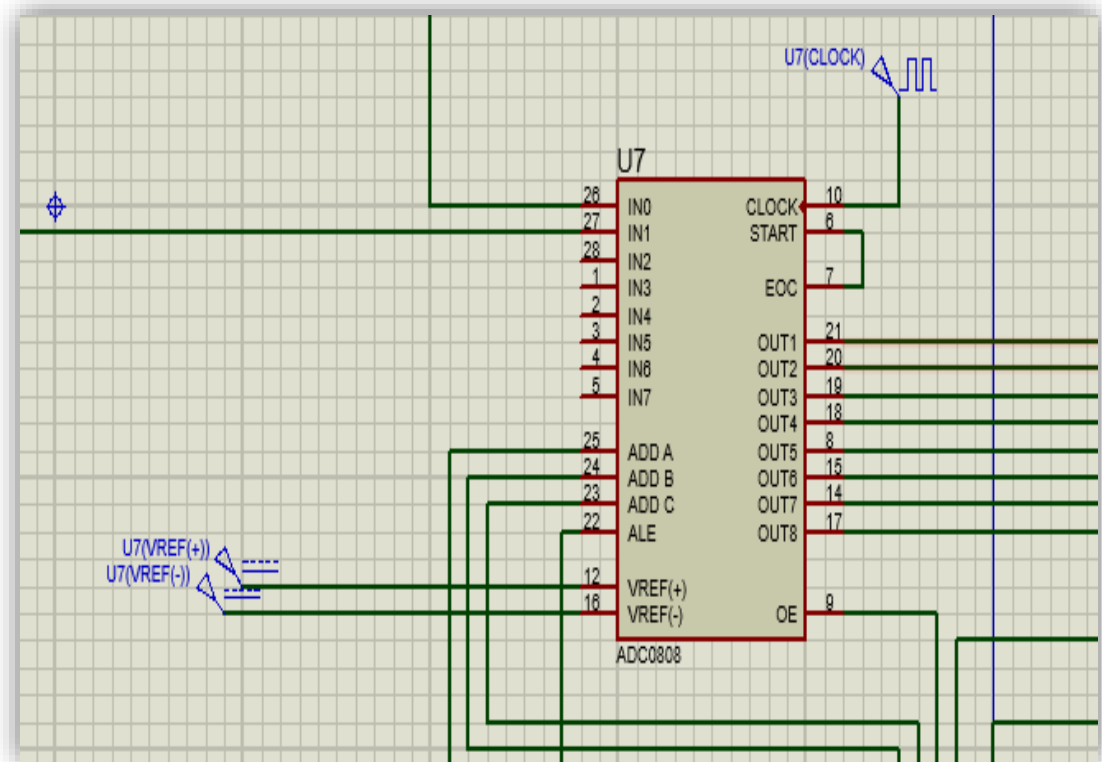


Figure5: ADC

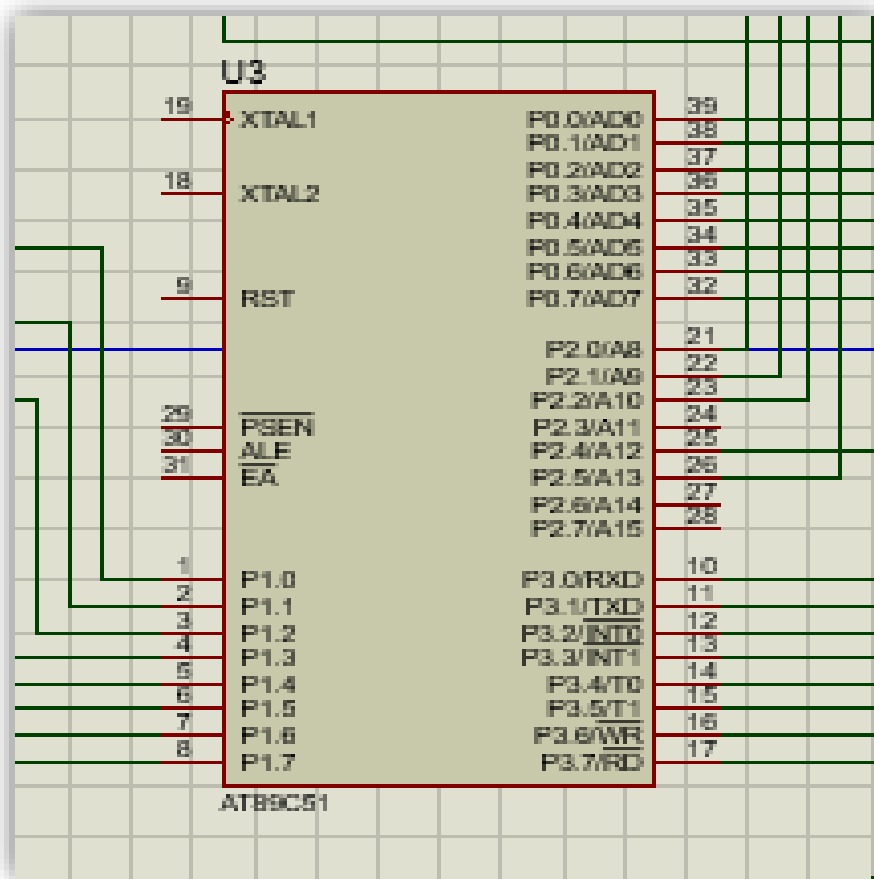


Figure 6: Microcontroller C8051F020

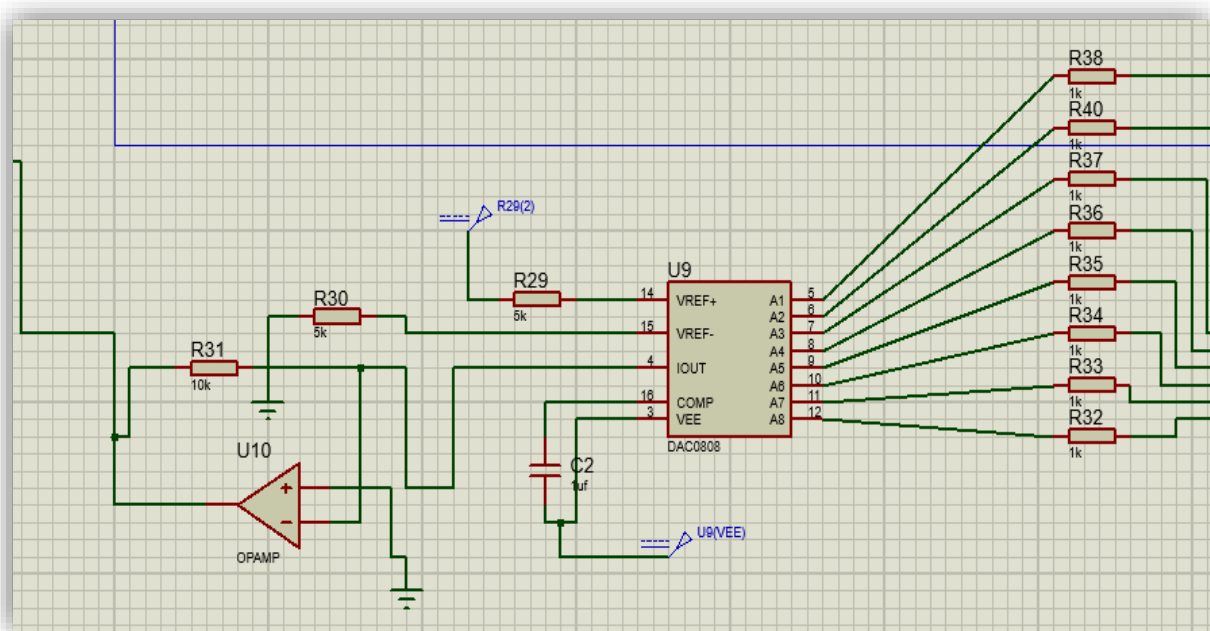


Figure 7: DAC

Output after DAC

- Without Filtration and Switch ON

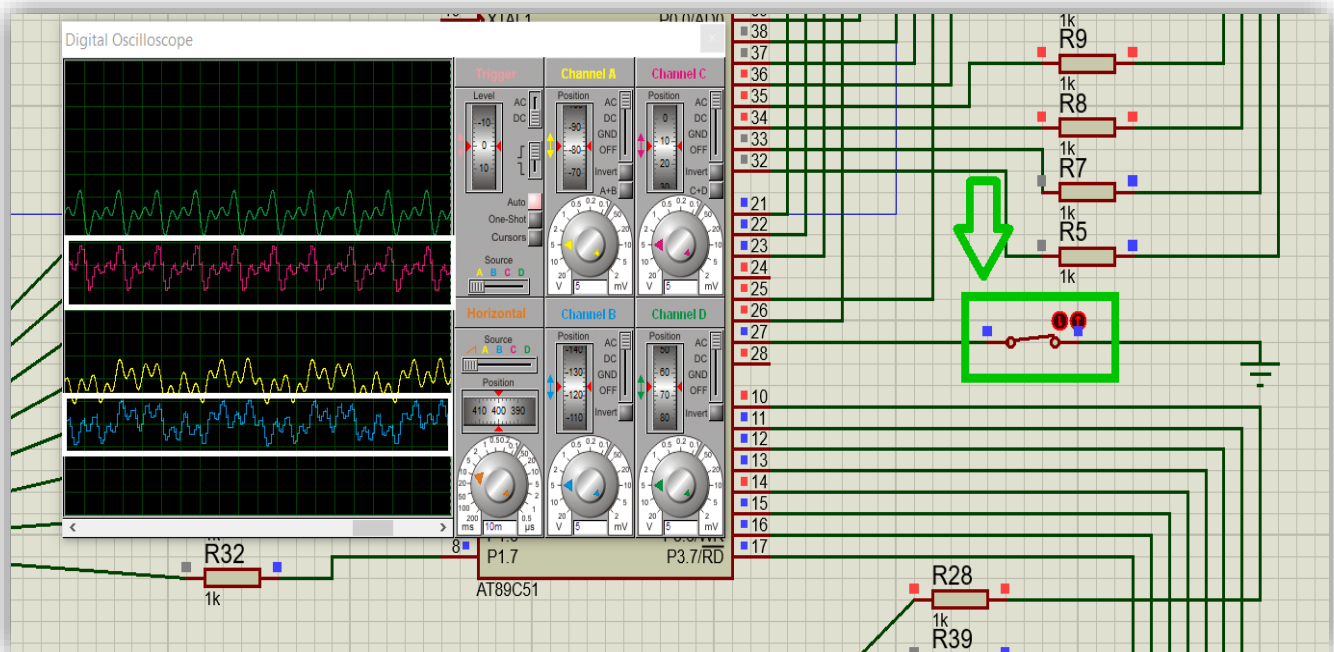


Figure8 :Output without Filtration

- With Filtration and Switch OFF

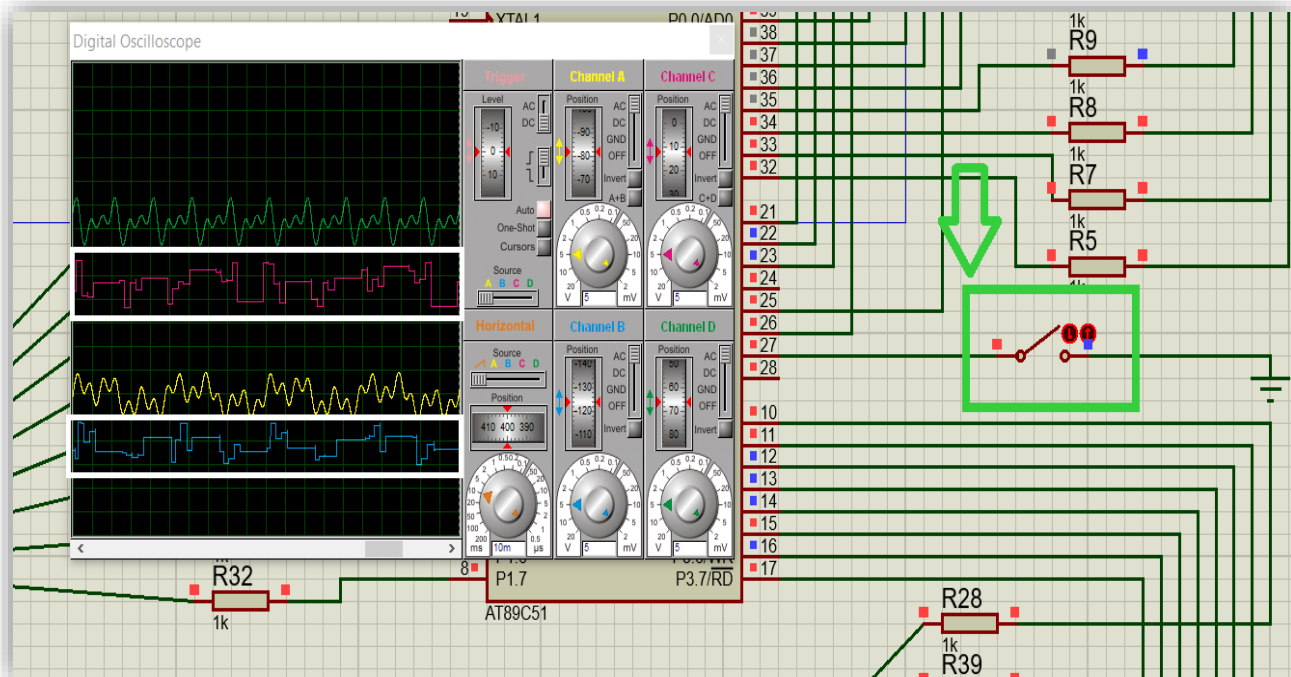


Figure9 :Output With Filtration

Description for Digital filters used along with equations

We use two types of filters :

1. Low Pass Filter for signal one
2. High Pass Filter for signal two

Filter order N=3

✚ Used Equation

$$y[n] = b_0 * x[n] + b * x[n-1] + + b * x[n-N]$$

$$y[n] = \sum_{i=0}^n b_i * x[n-i]$$

- $x[n]$ ----- input signal
- $y[n]$ ----- output signal
- b_i ----- filter co-efficients
- N ----- filter order

Figure 10 :Filtration Equations

✚ Used coefficients

Low Pass Filter	0.34917535	0.229359258	0.229359258	0.34917535
High Pass Filter	-0.641653637	-0.649742213	0.649742213	0.649742213

Figure 11 : Filtration Coefficients